

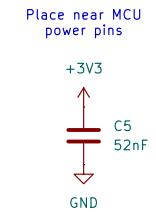


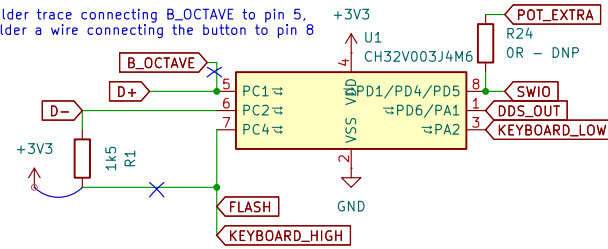Cut the solder trace connecting B_OCTAVE to pin 5, instead solder a wire connecting the button to pin 8



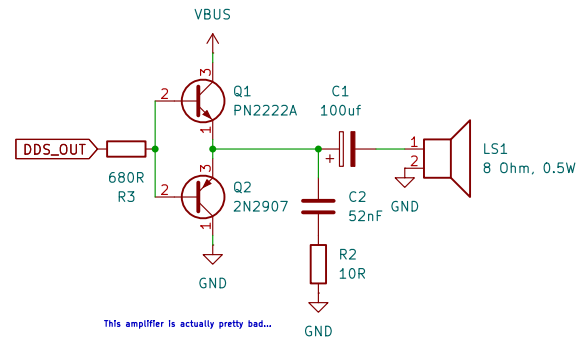Mistakes that made it to the production:
The resistor must be connected between 3v3 and PC2 instead
(this can be fixed on board by connecting the upper leg of the resistor to left pin of a C5 instead)



This amplifier is actually pretty bad...

